

# Learning Experience F.3

Ethan Davidson and Patrick Rooney

ECE 2544

Fall 2024

# Design Changes

We did not make any changes to the function unit design from Learning Experience F.2 because our function unit from Learning Experience F.2 already had all of our desired functionality and was completely compatible with our branch on non-negative instruction we added in Learning Experience F.3. In the control unit, we made changes to the next\_pc mux to allow Branch On Non-Negative to change the Program Counter. We also added a branch adder circuit, which consists of sixteen full-adders, named branch\_adder module, to perform the arithmetic of the branch offset. This design change was necessary because our current design from Learning Experience F.2 could not support the performance of the branch offset needed in the branch on non-negative instruction. These were the only changes made in Learning Experience F.3.

## Opcodes

| Operation   | 15 | 14 | 13 | 12 | 11 | 10 | 9 | Function Select |   |   |   | MB | MD | RW | MW | PL | JB | BC |
|-------------|----|----|----|----|----|----|---|-----------------|---|---|---|----|----|----|----|----|----|----|
| Add         | 0  | 0  | 0  | 0  | 0  | 0  | 0 | 0               | 0 | 0 | 0 | 0  | 0  | 1  | 0  | 0  | 0  | 0  |
| Subtract    | 0  | 0  | 0  | 0  | 0  | 0  | 1 | 0               | 0 | 0 | 1 | 0  | 0  | 1  | 0  | 0  | 0  | 1  |
| Negative A  | 1  | 0  | 0  | 0  | 0  | 1  | 0 | 0               | 0 | 1 | 0 | 1  | 0  | 1  | 0  | 0  | 0  | 0  |
| Mult 4      | 0  | 0  | 0  | 1  | 0  | 1  | 1 | 1               | 0 | 1 | 1 | 0  | 0  | 1  | 0  | 0  | 0  | 1  |
| MovA        | 0  | 0  | 0  | 0  | 1  | 0  | 1 | 0               | 1 | 0 | 1 | 0  | 0  | 1  | 0  | 0  | 0  | 1  |
| Rem 8       | 0  | 0  | 0  | 1  | 1  | 0  | 0 | 1               | 1 | 0 | 0 | 0  | 0  | 1  | 0  | 0  | 0  | 0  |
| Nor         | 0  | 0  | 0  | 0  | 1  | 1  | 1 | 0               | 1 | 1 | 1 | 0  | 0  | 1  | 0  | 0  | 0  | 1  |
| Negative B  | 0  | 0  | 0  | 0  | 0  | 1  | 1 | 0               | 0 | 1 | 1 | 0  | 0  | 1  | 0  | 0  | 0  | 1  |
| Dec A       | 1  | 0  | 0  | 0  | 1  | 0  | 0 | 0               | 1 | 0 | 0 | 1  | 0  | 1  | 0  | 0  | 0  | 0  |
| NotA        | 1  | 0  | 0  | 0  | 1  | 1  | 0 | 0               | 1 | 1 | 0 | 1  | 0  | 1  | 0  | 0  | 0  | 0  |
| And         | 0  | 0  | 0  | 1  | 0  | 0  | 0 | 1               | 0 | 0 | 0 | 0  | 0  | 1  | 0  | 0  | 0  | 0  |
| Nand        | 0  | 0  | 0  | 1  | 0  | 0  | 1 | 1               | 0 | 0 | 1 | 0  | 0  | 1  | 0  | 0  | 0  | 1  |
| Not B       | 0  | 0  | 0  | 1  | 0  | 1  | 0 | 1               | 0 | 1 | 0 | 0  | 0  | 1  | 0  | 0  | 0  | 0  |
| ADD I       | 1  | 0  | 0  | 0  | 0  | 0  | 0 | 0               | 0 | 0 | 0 | 1  | 0  | 1  | 0  | 0  | 0  | 0  |
| SUB I       | 1  | 0  | 0  | 0  | 0  | 0  | 1 | 0               | 0 | 0 | 1 | 1  | 0  | 1  | 0  | 0  | 0  | 0  |
| NORI        | 1  | 0  | 0  | 0  | 1  | 1  | 1 | 0               | 1 | 1 | 1 | 1  | 0  | 1  | 0  | 0  | 0  | 1  |
| Negative B  | 0  | 0  | 0  | 0  | 0  | 1  | 1 | 0               | 0 | 1 | 1 | 0  | 0  | 1  | 0  | 0  | 0  | 1  |
| Decrement A | 1  | 0  | 0  | 0  | 1  | 0  | 0 | 0               | 1 | 0 | 0 | 1  | 0  | 1  | 0  | 0  | 0  | 1  |
| Not B       | 0  | 0  | 0  | 0  | 0  | 1  | 1 | 0               | 0 | 1 | 1 | 0  | 0  | 1  | 0  | 0  | 0  | 1  |
| BRNN        | 0  | 1  | 1  | 0  | 1  | 0  | 1 | 0               | 1 | 0 | 1 | 0  | 1  | 1  | 1  | 0  | 1  | 1  |

Figure 1.1 Opcode Table

# Simulation and Discussion

 


Figure 1.2 Annotated Simulation

 


Figure 1.3 Simulation

 


Figure 1.4 annotated BRNN simulation

In our annotated simulation, shown in *Figure 1.2*, the purple highlighter is instruction memory and the yellow highlighter is the program counter. When RA contains a value less than zero nothing happens because it only branches on non-negative values of RA. When  $RA \geq 0$  and  $AD > 0$  it branches forward by the magnitude of AD. When  $RA \geq 0$  and  $AD < 0$  it branches backward by the magnitude of AD. When  $RA \geq 0$  and  $AD = 0$  it starts an infinite loop effectively terminating the program. All other functions of the program counter still work properly. In our figure 1.4, we annotated our simulation to include specific times when BRNN happens, the program control, the source register A, and the AD value of the branch offset. The last green highlighted area is when BRNN occurs twice at the end of the simulation which is why there are two annotations.